



AMERICAN INTERNATIONAL UNIVERSITY – BANGLADESH (AIUB)

Faculty of Engineering

Bachelor of Science in Electrical and Electronic Engineering

EEE4227: Power System Protection (Section: D)

Summer 2020-2021

Total Marks: 40

Total time: 2 Hrs. + 10 Min (for pdf preparation + upload)

Final Assessment

Instructions:

- Write answers of all the questions in A4 paper/exercise book with **Pen only**.
- All the Questions corresponds to CO2.
- Upon completing this 'Take Home Exam', create a PDF having all of your answers.
- Rename the PDF file according to this format: "FA-ID" (Example: **FA-17-32749-2.pdf**)
- Upload the PDF file in the specific link on/before the deadline.
(find the link in MS Teams during exam period)

1. Evaluate the time-current grading scheme for the following power system model. The CT ratio is given as 200/5A. The load margin for the relay at different bus is considered to be 25%. (Use logical assumption if needed) [10]

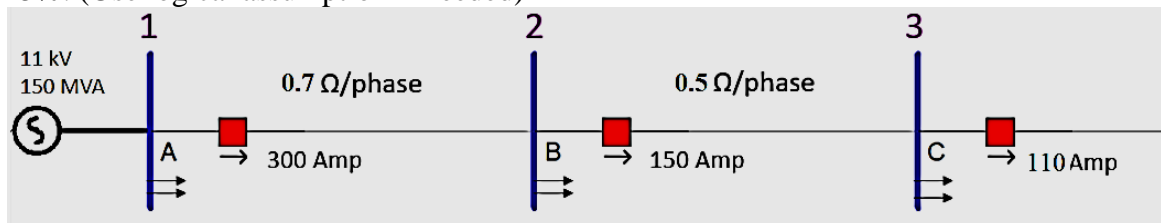


Figure for question no 1

2. (a) From the question given in 1, determine the numerical values of TCC curve of relay B. [5]
- (b) In a biased differential protection scheme as shown in figure 2(b), the current I_1 and I_2 is given as 300A and 290A respectively during a fault inside the winding under protection. CT ratio is given as $K=0.1$. The relay pick-up current is 2.5A. The slope of this relay system is given as 0.05. Identify whether the relay will operate or not? Justify your answer. [5]

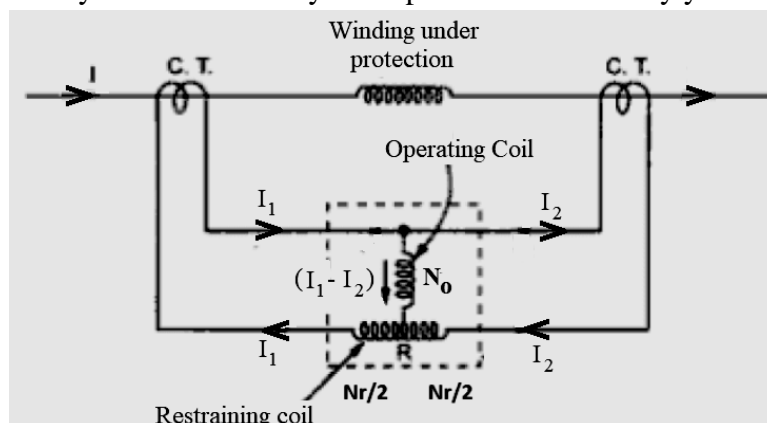


Figure for question no 2(b)

3. (a) The neutral point of an alternator of an 11 kV alternator is earthed through 15Ω resistance. The current transformers have ratio of 1000/5A. The relay is set to operate when there is an out of balance of current of 1.8 A. [5]
- (i) What percentage of winding is protected against L-G fault?
 - (ii) What must be the minimum value of earthing resistance to ensure 95% protection to each phase winding of the alternator?
- (b) How does the driving torque of an induction type directional relay change in proportional to the instantaneous active power value? (draw proper figure/vector if needed) [5]
4. (a) A 3-phase transformer of 0.44/11kV line voltage is connected in Y- Δ combination. The current transformers on 0.44kV side have current ratio of 800/5A. Identify the CT current ratio on 11 kV side of the main transformer? Given that, the line current of Y connected side of the main transformer is 400A. [5]
- (b) With proper circuit diagrams, describe the operating principle of distance protection using impedance relay. [5]